


## 2

# Operational Amplifiers

## 4 Active Circuits
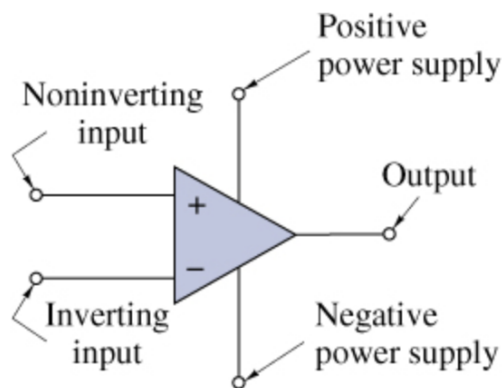
### 4.3 The Operational Amplifier


- Op Amps first used in a 1947 National Defence Research Council paper describing high gain amplifier circuits used to carry out mathematical operations.
  - Early op amps were made from vacuum tubes, but by the 70's, the IC version became dominant.



The global KCL equation for the complete set of variables is  $i_O = I_{C+} + I_{C-} + i_P + i_N$

- Transfer characteristic is divided into three regions or modes: +saturation, -saturation, and linear.
  - +Saturation mode when  $A(v_p - v_n) > V_{CC}$  and  $v_O = +V_{CC}$
  - -Saturation mode when  $A(v_p - v_n) < -V_{CC}$  and  $v_O = -V_{CC}$
  - Linear mode when  $A|v_p - v_n| < V_{CC}$  and  $v_O = A(-v_p - v_n)$
- The  $i - v$  relationships of the ideal model of the op amp are as:
  - $v_P = v_N$
  - $i_P = i_N = 0$

### Non-Inverting OP AMP

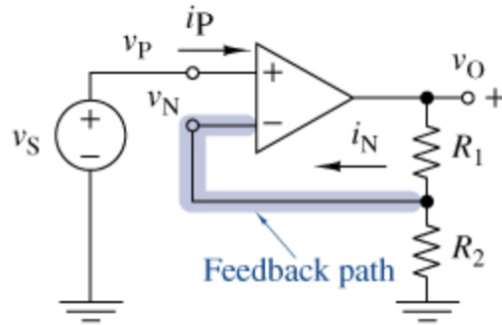


$$v_O = \frac{R_1 + R_2}{R_2} v_S$$

- The proportionality constant  $K$  is sometimes called the closed-loop gain because it defines the input-output voltage relationship when the feedback loop is connected (closed).
- There are two types of gains when discussing OP AMP circuits, first is closed-loop gains above.
  - Second is open-loop gain voltage gain provided by the OP AMP device itself.
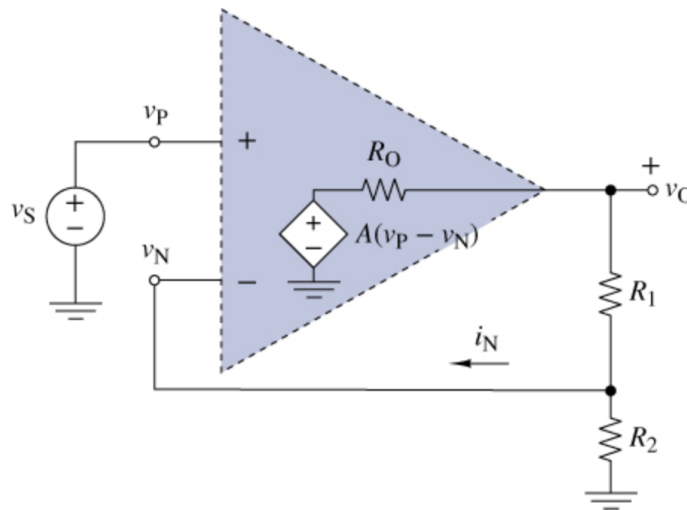
### Effects of Finite OP AMP Gain

- Ideal OP AMP model has infinite gain, but the actual devices have very large but finite gain.



Start by determining the output voltage

$$\begin{aligned}
 v_O &= \frac{R_1 + R_2}{R_O + R_1 + R_2} A(v_P - v_N) \\
 &= \left[ \frac{R_1 + R_2}{R_O + R_1 + R_2} \right] A \left[ v_S - \frac{R_2}{R_1 + R_2} v_O \right] \\
 &= \frac{A(R_1 + R_2)}{R_O + R_1 + R_2(1 + A)} v_S
 \end{aligned}$$

Now we take  $A \rightarrow \infty$

$$v_O = \frac{R_1 + R_2}{R_2} v_S = K v_S$$

## 4.4 OP AMP Circuit Analysis


- OP AMP circuit analysis uses advantage of OP AMPS being connected in cascade (like in series)

### Voltage Follower

- Also called a buffer
- Feedback is a direct path to the inverting input
- Since there is no input current  $i_P = 0$  there is no voltage across  $R_S$  and thus  $v_P = v_N$ 
  - Hence  $v_O = v_S$  and the name is the voltage “follower”
- This is used in interface circuits to separate the source from the load.

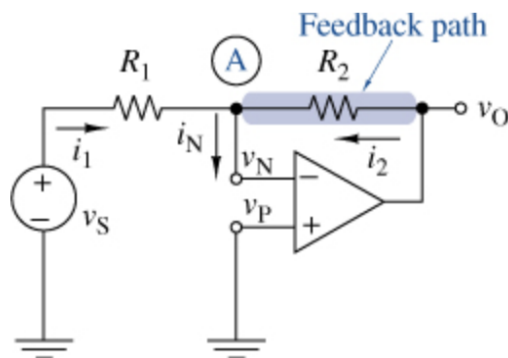
### The Inverting Amplifier

$$v_O = -\left(\frac{R_2}{R_1}\right) v_S$$



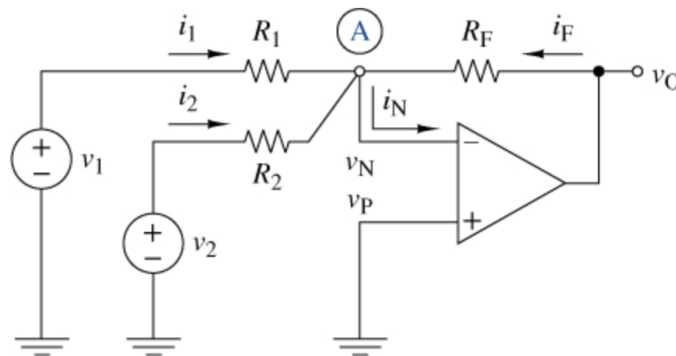
### The Summing Amplifier

$$v_O = \left( -\frac{R_F}{R_1} \right) v_1 + \left( -\frac{R_F}{R_2} \right) v_2$$



### The Differential Amplifier

$$v_O = \frac{R_2}{R_1} (v_2 - v_1)$$

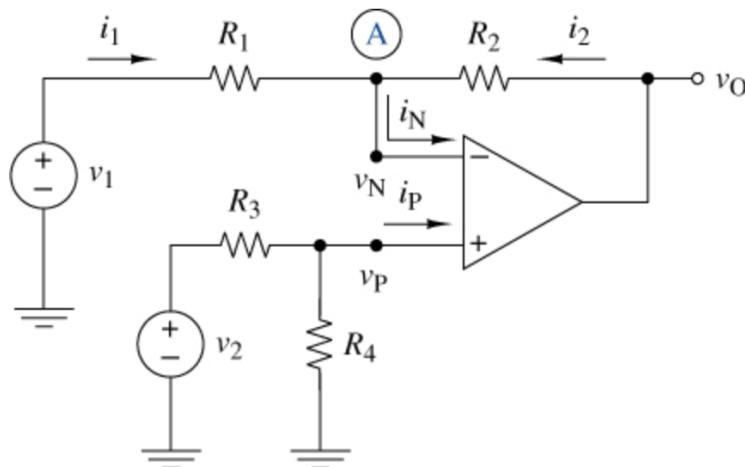

### Node-Voltage Analysis with OP AMP Circuits

1. Identify a node voltage at all non-reference nodes, including OP AMP outputs, but do not formulate node equations at the OP AMP output nodes.
2. Formulate node equations at the remaining non-reference nodes and then use the ideal OP AMP voltage constraint  $v_P = v_N$  to reduce the number of unknowns.